

SIMPLIFICATION OF LOGICAL FUNCTION USING KARNAUGH MAP (K-MAP):

Karnaugh Map (k-map) Introduction

- A Boolean expression may have many different forms.
- With the use of K-map, the complexity of reducing expression becomes easy and Boolean expression obtained is simplified.
- K-map also be said as **pictorial form** of truth table.
- K-map is alternative way of simplifying logic circuits.
- Instead of using Boolean algebra simplification techniques, you can transfer logic values from a Boolean statement or a truth table into a Karnaugh map (k-map)
- Tool for representing Boolean functions of up to six variables.
- K-maps are tables of rows and columns with entries represent 1's or 0's of SOP and POS representations.
- K-map cells are arranged such that adjacent cells correspond to truth rows that differ in only one bit position (*logical adjacency*)
- K-Map are often used to simplify logic problems with up to 6 variables
- **No. of Cells = 2^n , where n is a number of variables.**
- The Karnaugh map is completed by entering a '1' (or '0') in each of the appropriate cells.
- Within the map, adjacent cells containing 1's (or 0's) are grouped together in twos, fours, or eights and so on.

2 variable k-map

- For 2 variable k-map, there are $2^2 = 4$ input combinations.
- If A & B are two variables then;

SOP \rightarrow Minterms $\rightarrow A'B'$ ($m_0, 00$); $A'B$ ($m_1, 01$); AB' ($m_2, 10$); AB ($m_3, 11$)

POS \rightarrow Maxterms $\rightarrow A + B$ ($M_0, 00$); $A + B'$ ($M_1, 01$); $A' + B$ ($M_2, 10$); $A' + B'$ ($M_3, 11$)

➤ Mapping of SOP Expression:

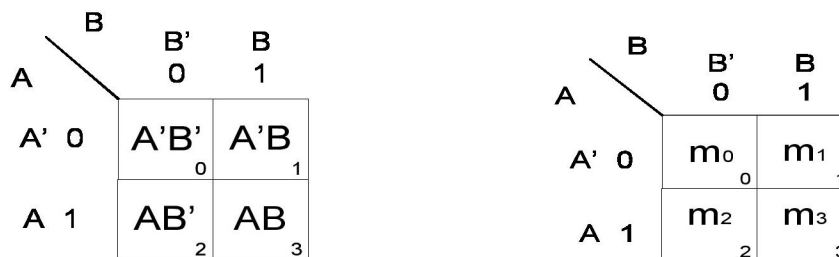



Fig. : Mapping of SOP form for two variable K-Map

- 1 in a cell indicates that the minterm is included in Boolean expression.
- For e.g. if $F = \sum m(0, 2, 3)$, then 1 is put in cell no. 0, 2, 3 as shown below.


		B	
		B'	B
A	0	1	0
	1	1	1

₀
₁
₂
₃

Ex. : Map for a 2-input OR gate.

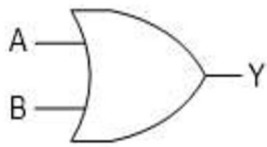

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

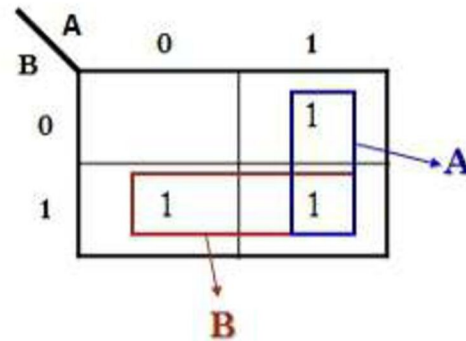

$$A + B$$

Ex. : Map for a 2-input EX-OR gate.

A	B	X
0	0	1 → $\bar{A}\bar{B}$
0	1	0
1	0	0
1	1	1 → AB

		\bar{B}	B
		\bar{A}	1
A	0	1	

$$F = A'B' + AB$$

➤ **Map following SOP expressions:**

Ex. : $F = AB$

Solution:

		B	
		B'	B
A	0	0	0
	1	0	1

₀
₁
₂
₃

Ex. : $F = AB' + A'B + A'B'$

Solution:

		B	
		B'	B
		0	1
A			
A' 0		1	1
		0	1
A 1		1	0
		2	3

Ex. : $F(A, B) = \sum(0, 2)$

Solution:

		B	
		B'	B
		0	1
A			
A' 0		1	0
		0	1
A 1		1	0
		2	3

Ex. : $F = m_0 + m_1$

Solution:

		B	
		B'	B
		0	1
A			
A' 0		1	1
		0	1
A 1		0	0
		2	3